

PHYSICS 142 HOMEWORK 4 SOLUTIONS

Q1) The force on a parallel plate capacitor = $\frac{1}{2} Q^2 \frac{d}{dx} \frac{1}{C}$ where

$C = \frac{A}{4\pi x} \Rightarrow F = \frac{1}{2} Q^2 \frac{4\pi}{A}$. Now we also know that the capacitor was charged by a battery of voltage $V \Rightarrow Q = C_0 V$ where C_0 is the initial capacitance where the separation between plates = d .

$$\Rightarrow Q = \frac{AV}{4\pi d} \Rightarrow F = \frac{2\pi}{A} \left(\frac{AV}{4\pi d} \right)^2 = \frac{AV^2}{8\pi d^2} \approx 1.7 \times 10^3 \text{ dynes}$$

$$\therefore F =$$

Now the work done externally = $\vec{F} \cdot \vec{L} = \frac{AV^2}{8\pi d} = 1.7 \times 10^3 \text{ ergs}$

Finally the electric field inside the plates = $E = 4\pi\sigma = \frac{4\pi Q}{A} = \frac{V}{2d}$

$$\therefore \text{energy stored} = \frac{1}{8\pi} E^2 A d = \frac{1}{8\pi} \frac{V^2}{4d^2} A d = \frac{1}{8\pi} \frac{V^2 A}{d}$$

So the electric field stores the same amount of energy as the external work done if the capacitor was to collapse on itself.

Q2) we have from Ohm's law $V = IR$

Now if ρ = resistivity of material, l is length of wire + ~~area~~

A = area of cross-section of the wire $\Rightarrow R = \frac{\rho l}{A}$

If there are n electrons per ^{cubic} centimeter & the drift velocity = v_d .

$\Rightarrow J = nev_d$ is the current density.

\therefore Current $I = JA = nev_d A$

$\therefore V = nev_d A \left(\frac{\rho l}{A} \right) = nev_d \rho l \Rightarrow v_d = \frac{V}{ne\rho l}$

$V = 6V = 2 \times 10^{-2}$ Stat volt

$n = 8 \times 10^{22}$ electron/cm³


$e = 4.8 \times 10^{-10}$ Stat Coul

$\rho = 1.7 \times 10^{-6}$ Ω cm

$l = 10^5$ cm

$\Rightarrow v_d = 2.5 \times 10^{-15}$ cm/s

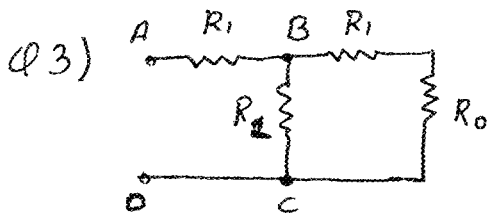\therefore time it takes to go a distance of 1 km = $\frac{10^5}{2.5 \times 10^{-15}} = 4 \times 10^{20}$ s



The equivalent resistance between BC = $\frac{(R_1 + R_0)R_1}{2R_1 + R_0}$

\therefore the total resistance = $R_1 + \frac{(R_1 + R_0)R_1}{(2R_1 + R_0)} = R_0$


~~$R_1 + \frac{(R_1 + R_0)R_1}{2R_1 + R_0} = \frac{2R_1 R_1 + R_0 R_1}{2R_1 + R_0}$~~ $\Rightarrow 2R_1^2 + 2R_1 R_0 + R_1^2 = 2R_1 R_0 + R_0^2$

$\Rightarrow R_0^2 = 3R_1^2 \Rightarrow R_1 = (\sqrt{3})^{-1} R_0 = R_0/\sqrt{3}$




Q4) We have 3 terminals a, b, c & resistors x, y, z.

Case analysis:

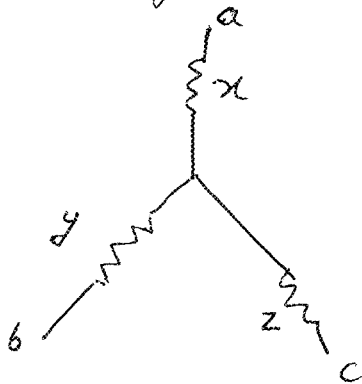- 1) If one terminal has three wires connected to it there are no remaining wires to create a potential drop across the other two terminals.
- 2) If all have only one wire connected to ~~the~~ each terminal then the only possibility is that they all meet at a point.



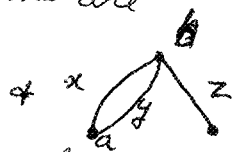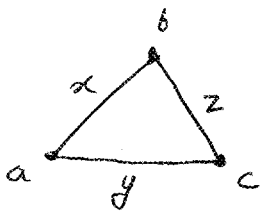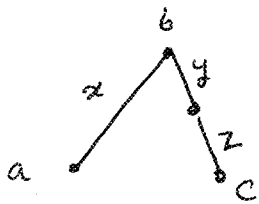- 3) The only remaining case is when there are two wires connected to at least one terminal. So possible diagrams are




& third

where the first diagram


is possible with a permutation of a, b, c.

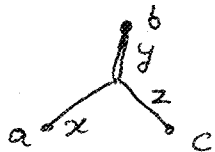Now if we consider the first possible case.



$$\begin{aligned} \Rightarrow R_{ab} = x + y = 30 \\ R_{ac} = x + z = 60 \\ R_{bc} = y + z = 70 \end{aligned} \Rightarrow z - y = 30 \left. \begin{array}{l} \Rightarrow 2z = 100 \\ \Rightarrow z = 50 \end{array} \right\} \begin{aligned} \Rightarrow y = 20 \\ \Rightarrow x = 10 \end{aligned}$$

2nd possible diagram.

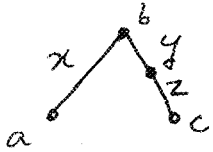

$$R_{ab} = x = 30$$


$$R_{bc} = y + z = 60$$

$$R_{ac} = x + y + z = 70$$

Impossible as $y+z=40$ using the first & 3rd equation.

as R_{ac} is the maximum drop the other permutations also does not work.

3rd possible diagram.

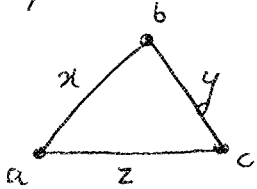

$$R_{ab} = \frac{x(y+z)}{x+y+z} = 30$$

$$R_{bc} = \frac{y(x+z)}{x+y+z} = 60$$

$$R_{ac} = \frac{z(x+y)}{x+y+z} = 70$$

$$\Rightarrow \frac{(y-x)z}{(x+y+z)} = 30$$

$$\Rightarrow \frac{y-x}{y+x} = \frac{3}{7}$$

$$\Rightarrow 7y - 7x = 3x + 3y$$

$$\Rightarrow 4y = 10x \Rightarrow 2y = 5x$$

Also we have $\frac{(z-y)x}{x+y+z} = 10$


$$\Rightarrow \frac{z-y}{z+y} = \frac{1}{3} \Rightarrow 3z - 3y = z + y$$

$$\Rightarrow 2z = 4y \Rightarrow z = 2y = 5x$$

$$\Rightarrow \frac{x(\frac{5}{2}x + 25x)}{x + \frac{5}{2}x + 5x} = 30 \Rightarrow \frac{15x}{17} = 30 \Rightarrow x = 34$$

$$\therefore y = 85 \quad \& \quad z = 170$$

Forth Possible case.

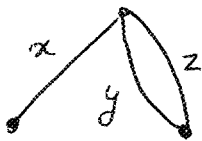


Is not possible as the sum of any of the potential is not equal to the third one.

So the only possible configurations are the ones listed in the question

There is no way of differentiating between the two diagrams from an external measurement.

Q5) The circuit is

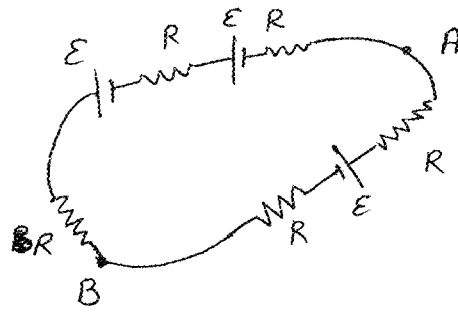

Let i be the current flowing through loop counterclockwise

$$\therefore i = \frac{3E}{5R} \quad \therefore \text{potential drop across AB} = 2E - 3iR = 2E - \frac{9E}{5} = \frac{E}{5}$$

To find the equivalent resistance between A+B we can neglect the batteries and treat the circuit purely as made up of resistors

$$\therefore R_{eq} = \frac{1}{\frac{1}{3R} + \frac{1}{2R}} = \frac{6}{5}R$$

$$\therefore \text{short circuit current} = \frac{E}{5} \cdot \frac{5}{6R} = \frac{E}{6R}$$

Another way to do this is to calculate the short circuit current first.

So short circuit current is the sum of the currents entering & leaving A or B

$$\text{Current entering A} = \frac{E}{2R}$$

$$\text{Current leaving A} = \frac{2E}{3R}$$

$$\therefore \text{net current through A} = \frac{E}{2R} - \frac{2E}{3R} = -\frac{1E}{6R}$$

$$\therefore R_{eq} = \frac{E_{eq}}{I_{sc}} = \frac{6R}{5}$$

So the theorem equivalent circuit has $\mathcal{E}_0 = E/5$ & $R_0 = 6R/5$

Q6) The charge initially = $Q = CV_0$

\therefore energy stored = $\frac{1}{2} CV_0^2 = \frac{1}{2} \frac{Q^2}{C}$ \therefore energy stored at time $t = \frac{1}{2} CV_0^2 e^{-2t/RC}$

Now we know the current ~~dissepatat~~ $I = \frac{V_0}{R} e^{-t/RC}$

\therefore energy dissepate at time $I = \frac{V_0^2}{R} e^{-2t/RC}$

\therefore total energy lost = $\int_0^{\infty} \frac{V_0^2 e^{-2t/RC}}{R} dt = \frac{V_0^2}{R} \frac{e^{-t/RC}}{(-2/RC)} \Big|_0^{\infty} = \frac{1}{2} \frac{V_0^2}{R} RC = \frac{1}{2} CV_0^2$

To show energy lost in time T we have


$$E = \int_0^T \frac{V_0^2 e^{-2t/RC}}{R} dt = \frac{1}{2} V_0^2 C (1 - e^{-2T/RC})$$

and using our initial value of energy + energy stored in the capacitor at time T we have energy lost by capacitor

$$= \frac{1}{2} CV_0^2 - \frac{1}{2} CV_0^2 e^{-2T/RC}$$

the same as that dissepated

through the resistor.

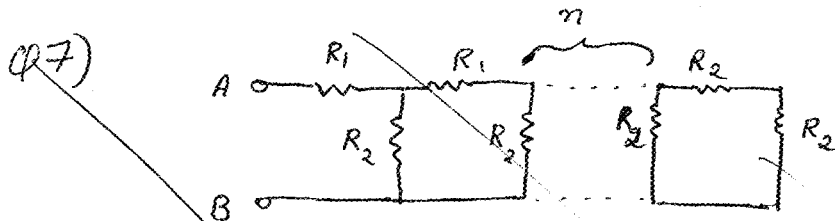


Let i_n be the current entering the n th R_1 resistor. ~~Let i_n be the current entering the~~ Therefore the current entering the n th R_2 resistor = $i_n - i_{n+1}$

D7) Let R be the equivalent resistance of the entire infinite chain of resistors.

\therefore Now consider stripping off the initial R_1 & R_2 and treating the rest of the resistors as R . As the chain is infinite removing any finite number of R_1 's & R_2 's does not change the equivalent resistance of the remaining chain.

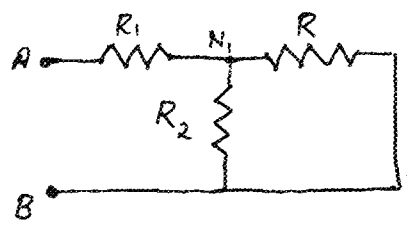
So if we treat the chain as $1R_1$ & $1R_2$ & $1R$ we have the circuit



has potential at $N_1 = V_0 - i_1 R_1$ where i_1 is the current through 1st R_1 . But as entire circuit has $R_{eq} = R$ $i_1 = \frac{V_0}{R}$

$$\therefore V_1 = V_0 - V_0 \left(\frac{R_1}{R} \right) = V_0 \left(\frac{R - R_1}{R} \right)$$

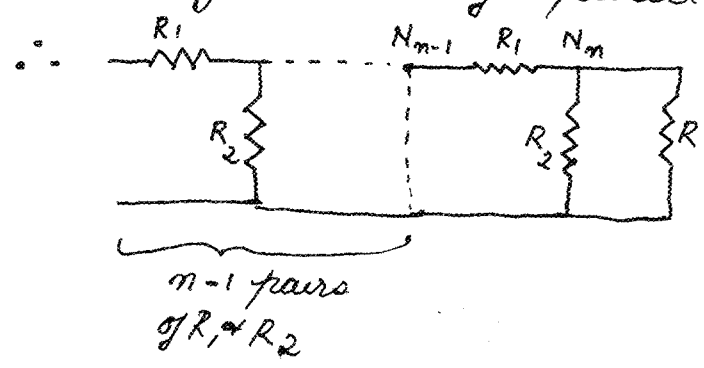Now let's consider n such pairs of R_1 & R_2 treated independently & the remaining chain being replaced by R .



Now using Thevenin's theorem we can replace the initial $n-1$ resistors' attenuation by the voltage source V_{n-1}

$$\therefore \text{current through } n\text{th } R_1 = \frac{V_{n-1}}{R_1} = i_n$$

$$\therefore \text{potential at } N_n = V_{n-1} - i_n R_1 = V_{n-1} \left(1 - \frac{R_1}{R} \right)$$

$$\Rightarrow V_n = V_{n-1} \left(\frac{R - R_1}{R} \right)$$

$$\therefore \text{we find that } V_n = V_0 \left(\frac{R - R_1}{R} \right)^n$$

Now we have also that $R = R_1 + \frac{RR_2}{R+R_2}$ using the first circuit

on the previous page $\Rightarrow R^2 + RR_2 = RR_1 + R_1R_2 + RR_2$

$$\Rightarrow R^2 - RR_1 - R_1R_2 = 0 \Rightarrow R = \frac{R_1 \pm \sqrt{R_1^2 + 4R_1R_2}}{2}$$

$$R > 0 \Rightarrow R = \frac{R_1 + \sqrt{R_1^2 + 4R_1R_2}}{2}$$

$$\Rightarrow V_n = V_0 \left(\frac{\sqrt{R_1^2 + 4R_1R_2} - R_1}{\sqrt{R_1^2 + 4R_1R_2} + R_1} \right)^n$$

\therefore The potential decrease as a geometric series.

Now if we want the sequence of potentials to go down by half

$$\left(\frac{\sqrt{R_1^2 + 4R_1R_2} - R_1}{\sqrt{R_1^2 + 4R_1R_2} + R_1} \right) = \frac{1}{2} \Rightarrow \sqrt{R_1^2 + 4R_1R_2} = 3R_1$$

$$\Rightarrow R_1^2 + 4R_1R_2 = 9R_1^2 \Rightarrow 4R_1R_2 = 8R_1^2 \Rightarrow R_1 = 0 \text{ or } R_2 = 2R_1$$

Clearly $R_1 = 0$ is not a solution so $R_2 = 2R_1 \Rightarrow R = 2R_1$

From our solution we can create such an attenuator to say the n^{th} power by replacing all the $n+1$ to infinite remain resistors by R .